

The Open University of Sri Lanka
Faculty of Engineering Technology
Department of Mechanical Engineering



085

Study Programme : Bachelor of Technology Honours in Engineering
Name of the Examination : Final Examination
Course Code and Title : DMX3304 Applied Electronics
Academic Year : 2021/22
Date : 16th February 2023
Time : 0930hr – 1230hr
Duration : **3 hours**

General Instructions

1. Read all instructions carefully before answering the questions.
 2. This question paper consists of **Eight (8)** questions in **Eight (8)** pages.
 3. Answer any **Five (5)** questions only. All questions carry equal marks.
 4. Answer for each question should commence from a new page.
 5. This is a Closed Book Test (CBT).
 6. Answers should be in clear handwriting.
 7. Do not use **Red** color pen.
-

Question 01

- a) Briefly explain the Kirchhoff's Current Law (KCL) and Kirchhoff's Voltage Law (KVL).

[4 Marks]

- b) Define the terms 'electric network' and 'electric circuit' used in electrical engineering.

[4 Marks]

- c) A Wheatstone bridge circuit has the resistances $R_{AB} = 60\Omega$, $R_{CD} = 60\Omega$, $R_{AD} = 40\Omega$, $R_{BC} = 40\Omega$, $R_{BD} = 100\Omega$ as given in Figure Q01(c). The supply is connected to points A and C. If the current drawn from the supply is 100mA, find the currents through R_{BC} , R_{CD} and R_{BD} .

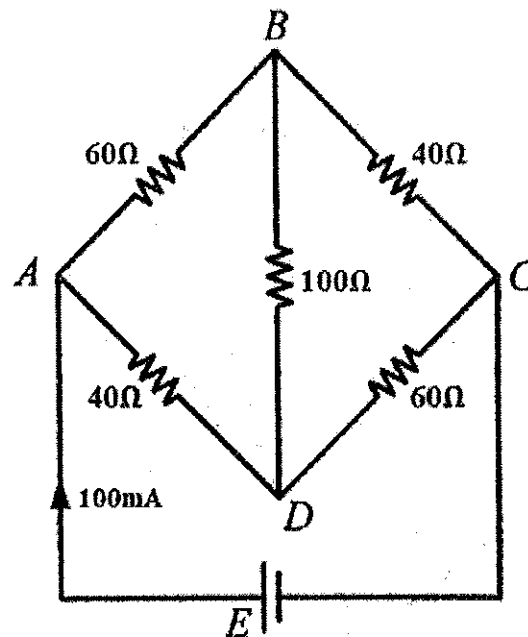


Figure Q01(c)

[6 Marks]

- d) Consider the circuit is given in Figure Q01(d), using KCL, KVL, and Ohm's law, Calculate:

i. I_1

[2 Marks]

ii. I_2

[2 Marks]

iii. V_o

[2 Marks]

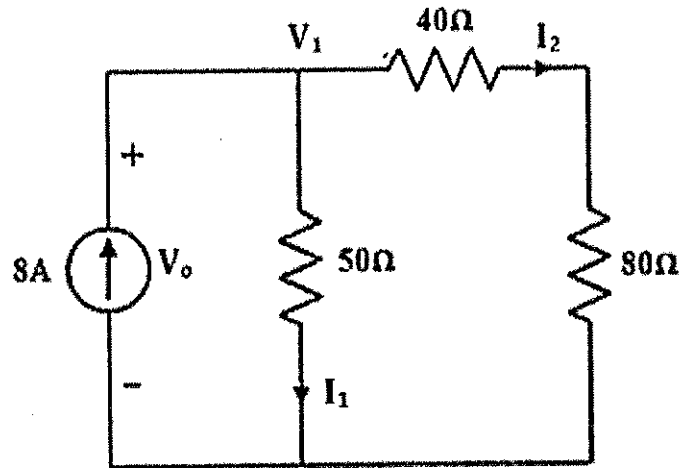


Figure Q01(d)

Question 02

a) Explain briefly why an ordinary junction transistor is called a Bipolar Junction Transistor (BJT). [3 Marks]

b) State three main advantages of using Field Effect Transistors (FET) in electronic designs. [3 Marks]

c) Consider the circuit given in **Figure Q02(c)**. Calculate the current I and the resistance between terminals A and B.

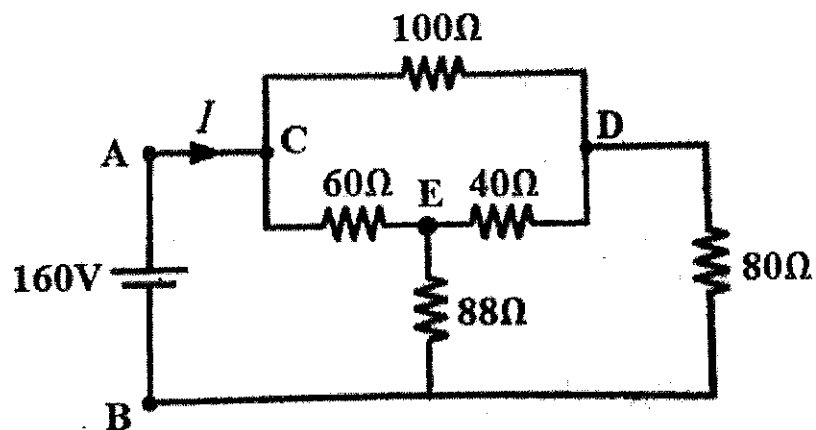


Figure Q02(c)

[6 Marks]

- d) Consider the JFET circuit given in **Figure Q02(d)**. Determine the value of drain current (I_D) for this circuit.

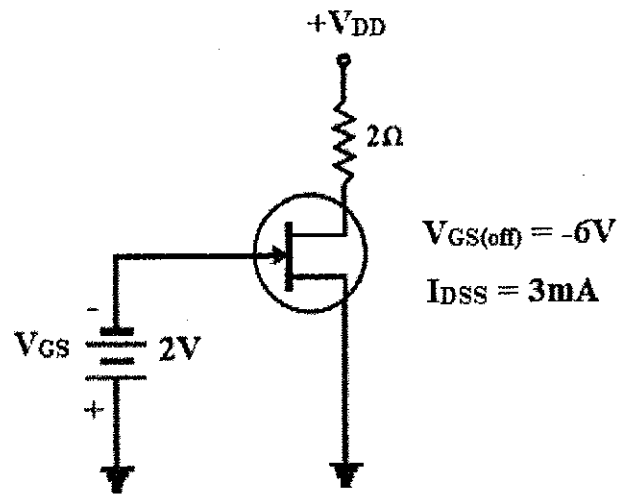


Figure Q02(d)

[8 Marks]

Question 03

- a) Briefly explain what is meant by the biasing of a transistor.

[3 Marks]

- b) State the definition of Current gain in the Common-Emitter (CE) configuration of a Bipolar Junction Transistor (BJT).

[3 Marks]

- c) Design a bias network circuit diagram for the BJT amplifier circuit given below in **Figure Q03(c)**, and calculate the values of,
(Assume the Common-emitter current gain is 150, $V_{BB} = 5\text{V}$ and $V_{BE} = 0.7\text{V}$)

- i. R
- ii. I_B
- iii. I_C
- iv. I_E

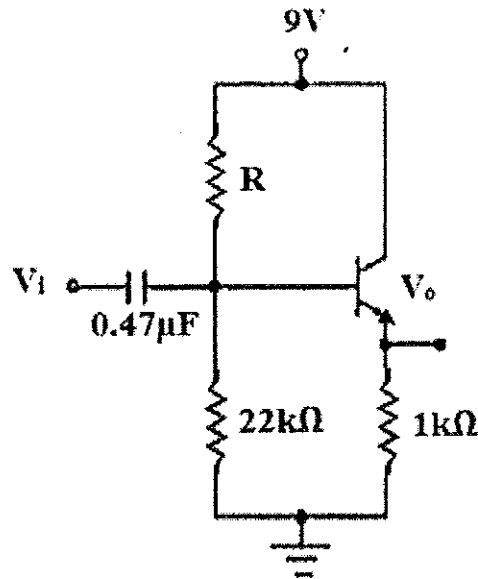


Figure Q03(c)

[14 Marks]

Question 04

- a) State 4 characteristics of an ideal Op-amp.

[4 Marks]

- b) Consider the Op-amp circuit that is shown in Figure Q04(b). If $V_i = 0.5V$, Calculate:

- The Output voltage V_o .
- The current through the $10k\Omega$ resistor.

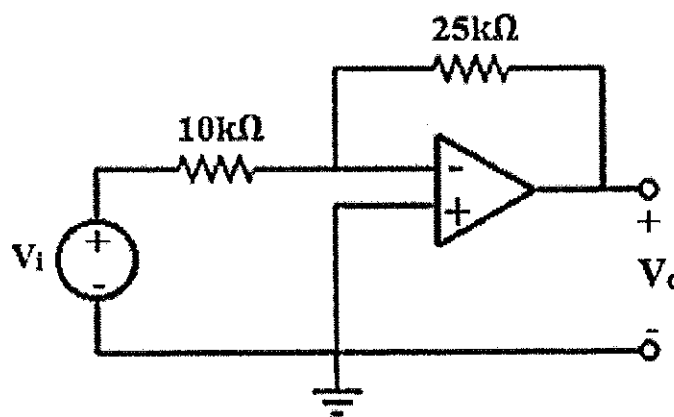


Figure Q04(b)

[6 Marks]

- c) Design a two-input summing amplifier that has a voltage gain of 10. You can follow the following steps to complete the design task.

Step 1 - Draw a two-input summing amplifier.

Step 2 - Determine the values of the resistors.

[10 Marks]

Question 05

- a) Draw circuit symbols of a normal diode and a Zener diode and sketch the V/I characteristics of both diodes.

[6 Marks]

- b) Consider the diode circuit that is shown in **Figure Q05(b)**. Use the Ideal diode model to calculate the current in both diodes and the Voltage at point D.

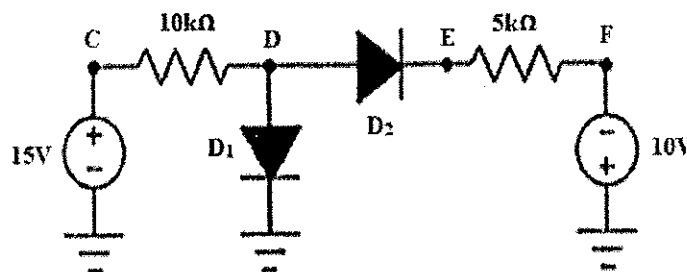


Figure Q05(b)

[8 Marks]

- c) Consider the Zener diode regulator that is shown in **Figure Q05(c)**. Determine V_L , V_R and I_Z .

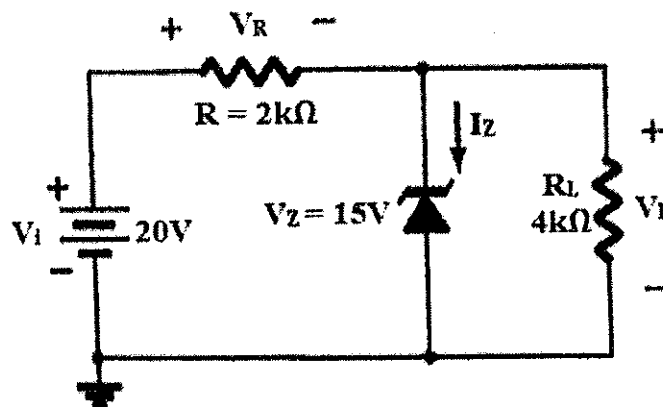


Figure Q05(c)

[6 Marks]

Question 06

- a) State three main differences between the Binary number system and the Decimal number system. [3 Marks]
- b) Convert the octal number 623_8 to Decimal, Binary and Hexadecimal number systems. [3 Marks]
- c) Represent the Decimal number -32_{10} as an 8-bit binary number using the **1's complement** and **2's complement representation**. [5 Marks]
- d) Represent the Decimal number 13597_{10} in Binary Coded Decimal (**BCD**). [4 Marks]
- e) Reduce the following Boolean expression to **THREE** literals.

$$(X'Y' + Z)' + Z + XY + WZ$$

[5 Marks]

Question 07

- a) State the De'-Morgan's theorem. [2 Marks]
- b) Simplify the following Boolean expression to **THREE literals** and construct the logic gate diagram and truth table for the simplified expression.

$$F = XY'Z + X'Y'Z + W'XY + WX'Y + WXY$$

[7 Marks]

- c) Simplify the Boolean expression given below using a **4 Variable K-Map**.

$$F = B'D + A'BC' + AB'C + ABC'$$

[3 Marks]

- d) Simplify the following Boolean expression using a **4 Variable K-Map** and express the function as,

$$F = AC' + B'D + A'CD + ABCD$$

- i. Sum of Products (SOP)
- ii. Product of Sums (POS)

[8 Marks]

Question 08

A building has four floors with staircases, and the staircase lights can be switched on or off at any floor when the switch on that floor is operated. Design a logic circuit for this case using the minimum number of gates. Show the design steps clearly. If the lights are controlled through a relay, show a suitable circuit that meets the above functional requirement. State any assumptions you make.

[20 Marks]

END