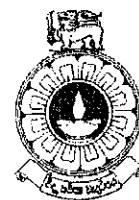


The Open University of Sri Lanka  
Faculty of Engineering Technology  
Department of Electrical & Computer Engineering

055




Study Programme	: Bachelor of Technology Honours in Engineering
Name of the Examination	: Final Examination
<b>Course Code and Title</b>	<b>: EEX6450 Analog Electronic Systems &amp; Instrumentation</b>
Academic Year	: 2021/2022
Date	: 28 <sup>th</sup> February 2023
Time	: 1330-1630 hrs
Duration	: <b>3 hours</b>

### General Instructions

1. Read all instructions carefully before answering the questions.
  2. This question paper consists of **Five (5)** questions in **Four (4)** pages.
  3. Answer **All** the questions.
  4. Answer for each question should commence from a new page.
  5. Relevant charts are provided.
  6. This is a Closed Book Test (**CBT**).
  7. Answers should be in clear hand writing.
  8. Do not use red colour pens.
-

Q1. Consider the circuit in the Figure-Q1 with Si transistors.

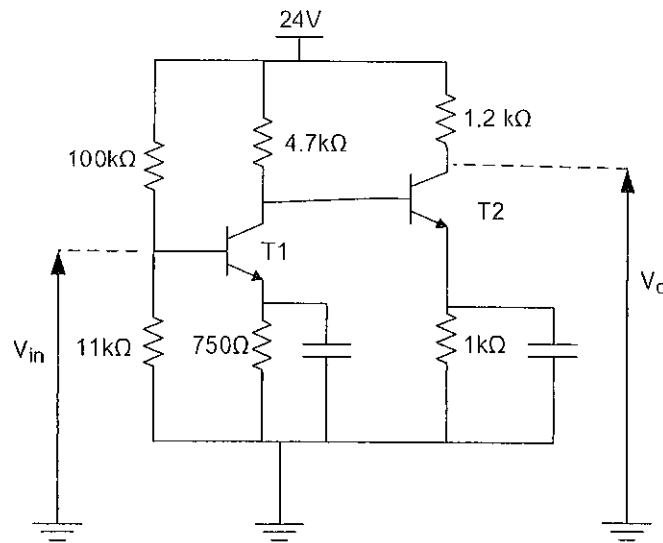


**Figure-Q1**

**T1:**  $\beta = h_{fe} = 100$ ,  $h_{ie} = 1k\Omega$       **T2:**  $\beta = h_{fe} = 60$ ,  $h_{ie} = 1.4k\Omega$   
 You may assume that the effect from  $h_{oe}$  and  $h_{re}$  are negligible.

- Find the quiescent values of  $V_{CE1}$ ,  $I_{C2}$ ,  $V_{C2}$  and  $V_{CE2}$ . (8 Marks)
- Draw the low frequency equivalent circuit. (6 Marks)
- Find the mid band voltage gain  $\frac{V_o}{V_{in}}$ . (6 Marks)

Q2. Consider the circuit diagram in Figure-Q2.

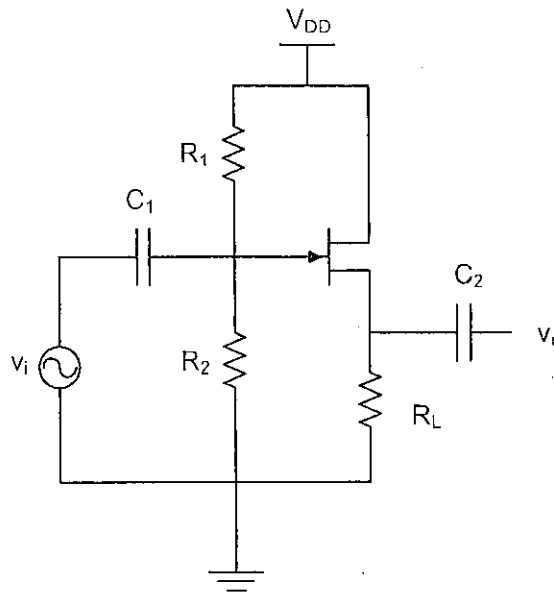


**Figure-Q2**

- Draw the high frequency equivalent circuit for the single stage amplifier shown in Figure-Q2. (7 Marks)

- (b) Clearly stating all your assumptions, find an expression for the voltage gain,  $A_v$ .  
(8 Marks)
- (c) Hence show that the low frequency voltage gain for this amplifier is  $\frac{\mu}{\mu+1}$ , where  
 $\mu = \frac{g_m}{g_d}$ .  
(5 Marks)

Q3.

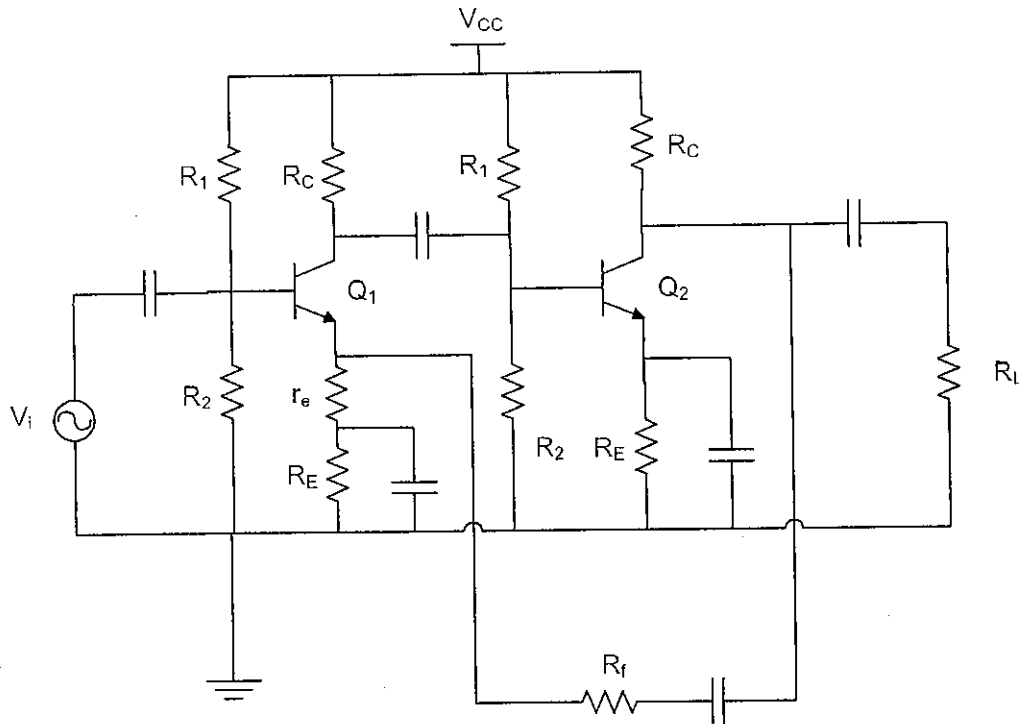


**Figure-Q3**

For the amplifier circuit shown in Figure-Q4,  $V_{CC} = 10\text{ V}$ ,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 2.2\text{ k}\Omega$ ,  $R_C = 3.6\text{ k}\Omega$ ,  $R_E = 1\text{ k}\Omega$ ,  $r_e = 100\Omega$ ,  $R_L = 10\text{ k}\Omega$  and  $R_f = 4.7\text{ k}\Omega$ . Both transistors Q1 and Q2 are identical and have  $h_{fe} = 100$ ,  $h_{ie} = 1.2\text{ k}\Omega$ .

- (a) Identify the type of feedback used. (2Marks)
- (b) Consider the circuit in Figure-Q3 without the feedback. Calculate the voltage gain and the input impedance. (10Marks)
- (c) Calculate the feedback ratio. (4Marks)
- (d) Hence calculate the overall voltage gain with feedback. (4Marks)

Q4.

- (a) Starting from the first principles, derive the Barkhausen criteria for oscillations to occur. (4Marks)
- (b) Stating all your assumptions, derive an expression for the feedback factor for the circuit in Figure-Q4. (4Marks)
- (c) Derive an expression for the forward gain. (6Marks)
- (d) Hence find the frequency of oscillation ( $C = 100\mu\text{F}$ ,  $L_1 = L_2 = 10\text{ mH}$ ,  $R_1 = R_2$ ). (6Marks)

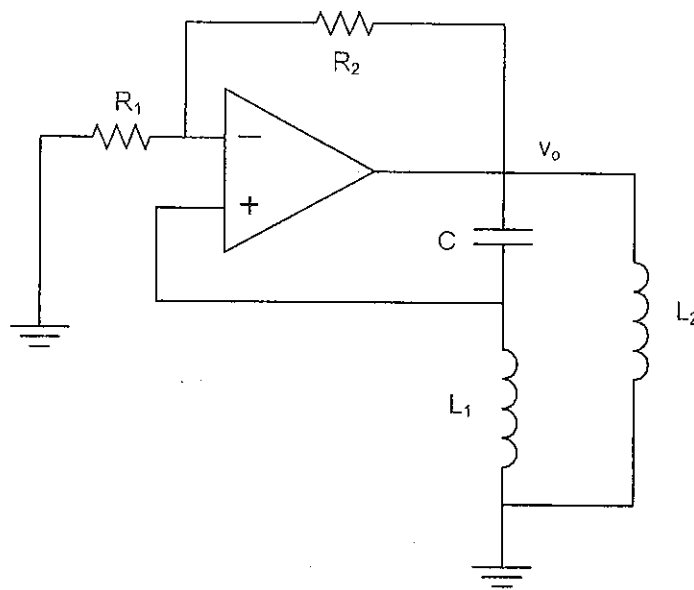

**Figure-Q4**

Q5.

- (a) A certain electronic medical thermometer has a frequency response given by  $\frac{2}{(1+j\omega)(1+3j\omega)}$ . Using a suitable frequency domain analysis, calculate the minimum time the doctor must wait after placing the thermometer on the patient, to have an accurate static reading. **(5 Marks)**
- (b) Derive the time domain behaviour of the above thermometer and justify your answer to (a). **(4 Marks)**
- (c) Above thermometer static reading taken on a patient in 20 different trials are given by 99.07, 99.54, 100.25, 100.24, 100.18, 99.50, 99.61, 99.86, 100.23, 99.94, 99.32, 100.48, 100.37, 99.90, 100.04, 100.04, 100.09, 100.39, 99.82, 100.79 Fahrenheit.
  - i. Determine how well the above readings fit to a random Normal distribution. **(3 Marks)**
  - ii. Determine the mean and the variance for the above Normal fit. **(4 Marks)**
  - iii. Hence, determine the accuracy of the above thermometer with a confidence level of 97%. **(4 Marks)**